

BEST AVAILABLE COPY

FIELDS and WAVES in MODERN RADIO

SIMON RAMO

*Vice President, Hughes Aircraft Company
Research Associate, California Institute of Technology*

JOHN R. WHINNERY

*Professor of Electrical Engineering
University of California*

SECOND EDITION

**JOHN WILEY & SONS, INC. NEW YORK
CHAPMAN & HALL, LTD. LONDON 1953**

SECOND EDITION

FOURTH PRINTING, OCTOBER, 1959

Copyright, 1944, 1953, by General Electric Company

All rights reserved. This book or any
part thereof must not be reproduced
in any form without the written permis-
sion of the publisher.

Library of Congress Catalog Card Number: 53-6615

Printed in the United States of America

5 IN MODERN RADIO

1-18

verified by differentiating:

$$1 \quad \frac{\partial V}{\partial z} = -\frac{1}{v} F' \left(t - \frac{z}{v} \right) \quad (4)$$

$$1 \quad \frac{\partial^2 V}{\partial z^2} = \frac{1}{v^2} F'' \left(t - \frac{z}{v} \right)$$

derivatives with respect to the entire
ing the two equations (4), (1) is

that is meant by the statement that
This may be done by recognizing that
rence value of the function (i.e., keep
ument, $t - (z/v)$, a constant. This
e positive z direction with velocity v

$$- \frac{z}{v} = K \quad (5)$$

1 degree differential equation has been
e written as any function of $t + (z/v)$
similar to those used for the first solu-
e traveling in the negative z direction
lution to (1) is then

$$- \frac{z}{v} + F_2 \left(t + \frac{z}{v} \right) \quad (6)$$

$\cos \omega[t - (z/v)]$, $e^{j\omega[t - (z/v)]}$, and $[t + (z/v)]^2$ to

$[t - (z/v)]$ versus $\omega z/v$ for values of $\omega t = 0$,
nonstrates the interpretation as a propagating

AGE AND CURRENT IN THE IDEAL LINE

developed above, Eq. 1-17(6), is sub-
e equation, 1-16(3),

$$1 \quad \left(t - \frac{z}{v} \right) + \frac{1}{v} F_2' \left(t + \frac{z}{v} \right) \quad (1)$$

1-19

OSCILLATION AND WAVE FUNDAMENTALS

27

This expression may be integrated partially with respect to t :

$$I = \frac{1}{Lv} \left[F_1 \left(t - \frac{z}{v} \right) - F_2 \left(t + \frac{z}{v} \right) \right] + f(z) \quad (2)$$

If this result were substituted in the other transmission line equation,
1-16(4), it would be found that the function of integration, $f(z)$, could
only be a constant. But we are not interested in possible superposed
d-c solutions in studying the wave solution, so this will be ignored.
Equation (2) may then be written

$$I = \frac{1}{Z_0} \left[F_1 \left(t - \frac{z}{v} \right) - F_2 \left(t + \frac{z}{v} \right) \right] \quad (3)$$

where

$$Z_0 = Lv = \sqrt{\frac{L}{C}} \quad (4)$$

The constant Z_0 as defined by (4) is called the *characteristic imped-*
ance of the line, and is seen from (3) to be the ratio of voltage to current
for a single one of the traveling waves at any given point and given
instant. The negative sign for the negatively traveling wave would
of course be expected since the wave propagates to the left, and by our
convention current is positive if flowing to the right.

1-19 REFLECTION AND TRANSMISSION AT A DISCONTINUITY

Most transmission line problems are concerned with junctions
between a given uniform line and a line of different characteristic
impedance, a load impedance or some other element that introduces a
discontinuity. By Kirchhoff's laws, total voltage and current must
be continuous across the discontinuity. The total voltage in the line
may be regarded as the sum of voltage in a positively traveling wave,
equal to V_1 at the point of discontinuity, and a voltage in a reflected
or negatively traveling wave, equal to V_1' at the discontinuity. The
sum of V_1 and V_1' must be V_L , the voltage appearing across the load
impedance Z_L :

$$V_1 + V_1' = V_L \quad (1)$$

Similarly, the sum of currents in the positively and negatively traveling
waves of the line, at the point of discontinuity, must be equal to the
current flowing into Z_L :

$$I_1 + I_1' = I_L \quad (2)$$

By utilizing the relations between voltage and current for the two traveling waves as found in the preceding article, (2) becomes

$$\frac{V_1}{Z_0} - \frac{V_1'}{Z_0} = \frac{V_L}{Z_L} \quad (3)$$

By eliminating between (1) and (3), the ratio of voltage in the reflected wave to that in the incident wave (*reflection coefficient*) and the ratio of the voltage in the load to that in the incident wave (*transmission coefficient*) may be found:

$$\rho = \frac{V_1'}{V_1} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (4)$$

$$\tau = \frac{V_L}{V_1} = \frac{2Z_L}{Z_L + Z_0} \quad (5)$$

The most interesting, and perhaps the most obvious, conclusion from the above relations is this: there is no reflected wave if the terminating impedance is exactly equal to the characteristic impedance of the line. All energy of the incident wave is then transferred to the load impedance, which cannot be distinguished from a line of infinite length and characteristic impedance $Z_0 = Z_L$.

Note that for arbitrary time functions the "impedance" used above should be a pure resistance in order for the ratio of instantaneous load voltage to instantaneous load current to be given by Z_L , as used above. The impedance form has, however, been utilized so that the equation will apply immediately to steady-state sinusoidal waves expressed in the complex form for later use.

PROBLEMS

1-19a For arbitrary time functions, assuming Z_L a pure resistance, find the fraction of the incident power reflected, and the fraction of the incident power transmitted to Z_L .

1-19b Calculate the reflection coefficient, transmission coefficient, and the power quantities of Prob. a for $Z_L = 0$, $\frac{1}{2}Z_0$, Z_0 , $2Z_0$, and ∞ .

1-20 SOME SIMPLE PROBLEMS ON TRAVELING WAVES

A. *D-C Voltage Applied to an Infinite Line.* Consider the case of a d-c voltage V , suddenly applied to an ideal line of infinite length (Fig. 1-20a). The line starts to charge to voltage V , the wave front traveling with the velocity $v = 1/\sqrt{LC}$. Since there is never any discontinuity, there is never any reflected wave, and the only current is

en voltage and current for the two preceding article, (2) becomes

$$\frac{V_1'}{Z_0} = \frac{V_L}{Z_L} \quad (3)$$

3), the ratio of voltage in the reflected wave (reflection coefficient) and the ratio of in the incident wave (transmission

$$\frac{V_1'}{V_1} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (4)$$

$$\frac{I_1'}{I_1} = \frac{2Z_L}{Z_L + Z_0} \quad (5)$$

perhaps the most obvious, conclusion there is no reflected wave if the terminal to the characteristic impedance of incident wave is then transferred to the be distinguished from a line of infinite length $Z_0 = Z_L$.

functions the "impedance" used above order for the ratio of instantaneous load current to be given by Z_L , as used above. ver, been utilized so that the equation dy-state sinusoidal waves expressed in

ons, assuming Z_L a pure resistance, find the ected, and the fraction of the incident power

coefficient, transmission coefficient, and the = 0, $\frac{1}{2}Z_0$, Z_0 , $2Z_0$, and ∞ .

ON TRAVELING WAVES

In Infinite Line. Consider the case of a lied to an ideal line of infinite length to charge to voltage V , the wave front $1/\sqrt{LC}$. Since there is never any reflected wave, and the only current is

that flowing in the positive wave, V/Z_0 . This then is a d-c current flowing to the charges which appear on the line as voltage moves along. At any time t after the voltage is impressed, there is voltage V and current V/Z_0 in the line up to the point $z = vt$, and no voltage or current beyond.

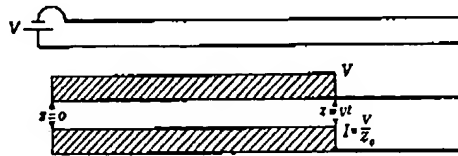


Fig. 1-20a Direct-current voltage suddenly applied to an infinite line.

B. D-C Voltage Applied to a Shorted Line. Suppose that the d-c voltage is applied to a line which is not infinite in length, but is shorted at some point, $z = l$ (Fig. 1-20b). We know that finally infinite current will flow if V is maintained. However, the mechanism of current build-up is interesting. After voltage is applied to the line, everything proceeds as in A until the time that the wave reaches the short

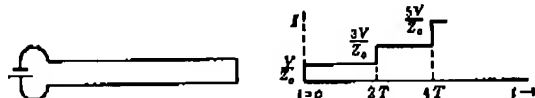


Fig. 1-20b Direct-current voltage suddenly applied to a shorted line.

circuit. At the time the incident wave with voltage V appears across the short circuit, which demands zero voltage, a reflected or negatively traveling wave of voltage $-V$ is sent back so that the sum of voltages in the two waves is indeed zero. Since current in the negative traveling wave is the negative of voltage divided by Z_0 , this is $-(-V/Z_0)$ or $+V/Z_0$ and so adds directly to the current in the positive traveling wave. This reflected wave then moves to the left, leaving a wake of zero voltage and a current equal to $2V/Z_0$ behind it. As soon as the reflected wave has traveled back to the source, it brings the zero voltage condition back to this point so that the d-c voltage must send out a new wave of voltage V down the line, with associated current V/Z_0 , making a total current in the line $3V/Z_0$ at this time. Current then builds up to infinity in the step manner indicated by Fig. 1-20b. T is the time l/v required for a wave to travel one way down the line.

C. Charged Line Connected to a Resistor. Consider an ideal line of length l initially charged to a d-c potential V , with a resistance R connected across the input at time $t = 0$.

The voltage across the resistance is the sum of the d-c voltage of the line and the voltage in the wave, V_1 :

$$V_R = V + V_1 \quad (1)$$

The current flowing into the resistor is merely the negative of current for the positively traveling wave:

$$I_R = -I_1$$

or

$$\frac{V_R}{R} = -\frac{V_1}{Z_0} \quad (2)$$

By combining (1) and (2),

$$V_R = V \left(\frac{R}{R + Z_0} \right) = -V_1 \frac{R}{Z_0} \quad (3)$$

For example, if $R = Z_0$, the voltage appearing across the resistance at the first instant is half the d-c voltage of the line, as is the voltage appearing in the traveling wave. When this wave reaches the open

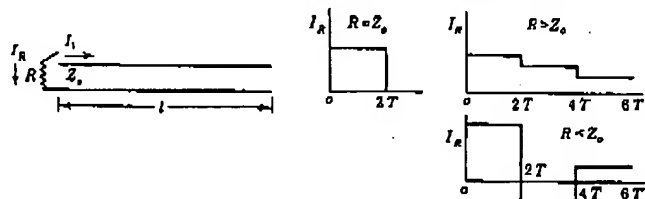


Fig. 1-20c. Charged line of length l suddenly connected to a resistor.

end, there must then be started a reflected wave such that total current is zero, so current in the reflected wave must be $-I_1$ or $V/2R$. Because current in the reflected wave is the negative of voltage divided by Z_0 , this will require a voltage $-V/2$ for the reflected wave. Thus in the case of $R = Z_0$, the original wave wipes out half the voltage, and the corresponding current, $-V/2Z_0$, is that which flows through R . The reflected wave wipes out the remaining half of the voltage and, of course, reduces current to zero. When this wave reaches $R = Z_0$ there is no further reflection, so all is still. Current wave shape is shown in Fig. 1-20c. Also shown are currents for $R > Z_0$ and $R < Z_0$.

PROBLEMS

1-20a An ideal line of length l is charged to d-c voltage V and shorted at its input at time $t = 0$. Sketch the current wave shape through the short as a function of time.

1-20b An ideal open-circuit voltage V suddenly applied at through the input source as a

1-21 IDEAL LINE WITH APP

Much of the preceding the type of variation with mission lines. Most prac least partially with sinuso sinusoidal in time is appli exponential (see Art. 1-11)

$V|$.

Then the corresponding po

Similarly, a negatively trav

Or the total solution, ma waves, is

$$V = e^{j\omega t}$$

The corresponding current,

$$I = \frac{e^{j\omega t}}{Z_0}$$

For problems in which we soidal quantities, it is not n each time, since it will alwa; plied by this factor; we rew

$$V = V$$

$$I = \frac{1}{Z}$$

where

$$\beta = \frac{\omega}{v}$$

The quantity β is called the p the instantaneous phase at a if voltage and current are ob exactly the same at points s

**This Page is Inserted by IFW Indexing and Scanning
Operations and is not part of the Official Record**

BEST AVAILABLE IMAGES

Defective images within this document are accurate representations of the original documents submitted by the applicant.

Defects in the images include but are not limited to the items checked:

- ☒ **BLACK BORDERS**
- ☐ **IMAGE CUT OFF AT TOP, BOTTOM OR SIDES**
- ☐ **FADED TEXT OR DRAWING**
- ☐ **BLURRED OR ILLEGIBLE TEXT OR DRAWING**
- ☐ **SKEWED/SLANTED IMAGES**
- ☐ **COLOR OR BLACK AND WHITE PHOTOGRAPHS**
- ☐ **GRAY SCALE DOCUMENTS**
- ☐ **LINES OR MARKS ON ORIGINAL DOCUMENT**
- ☐ **REFERENCE(S) OR EXHIBIT(S) SUBMITTED ARE POOR QUALITY**
- ☐ **OTHER: _____**

IMAGES ARE BEST AVAILABLE COPY.

As rescanning these documents will not correct the image problems checked, please do not report these problems to the IFW Image Problem Mailbox.